

Name: Key

Period: \_\_\_\_\_

Date: \_\_\_\_\_

Electricity: Capacitors Problems I


| SERIES  | PARALLEL                     |  |
|---|------------------------------|--|
| $\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$ | $C_T = C_1 + C_2 + \dots$    |  |
| $C = \frac{Q}{V}$                                       | $C = \epsilon_0 \frac{A}{d}$ | $U = \frac{1}{2} Q \Delta V = \frac{1}{2} C V^2$ |

I. Simplify the following electric circuits and answer the following.

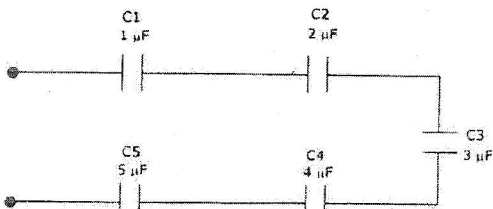1.

*Series*

$$\frac{1}{C} = \frac{1}{1} + \frac{1}{2} + \frac{1}{3} + \frac{1}{4} + \frac{1}{5}$$



$$\frac{1}{C} = \frac{60+30+20+15+12}{60} = \frac{137}{60}$$

$$\frac{1}{C} = \frac{60}{137} \quad C = \frac{60}{137} = 0.44 \mu F$$


Type of circuit: Series

Total Capacitance: 0.44 μF

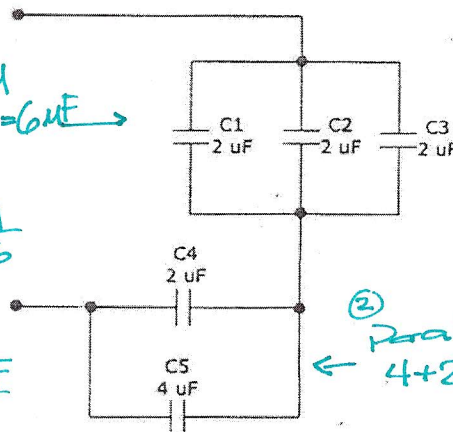2.

① Parallel  
 $2+2+2=6 \mu F$

③ Series  
 $\frac{1}{C} = \frac{1}{6} + \frac{1}{6}$   
 $\frac{1}{C} = \frac{2}{6}$   
 $C = \frac{6}{2} = 3 \mu F$




② Parallel  
 $4+2=6 \mu F$

Type of circuit: COMBINED

Total Capacitance: 3 μF

3.

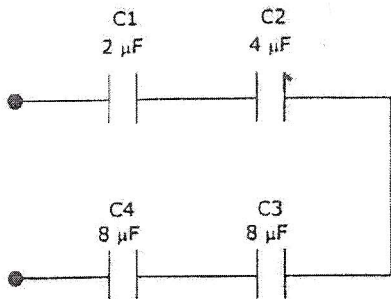

Type of circuit: Series

Total Capacitance: 1 μF


$$\frac{1}{C} = \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{8}$$

$$\frac{1}{C} = \frac{4+2+1+1}{8} = \frac{8}{8}$$

$$C = 1 \mu F$$

4.

② Parallel  
 $C_T = 2+2$   
 $C_T = 4$

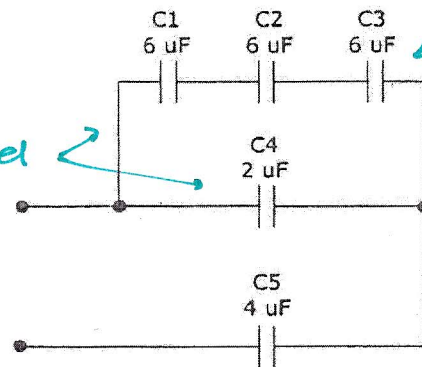

① Series  
 $\frac{1}{C} = \frac{1}{6} + \frac{1}{6} + \frac{1}{6}$   
 $\frac{1}{C} = \frac{3}{6}$   
 $C = \frac{6}{3} = 2 \mu F$

③ Series  
 $\frac{1}{C_T} = \frac{1}{4} + \frac{1}{4}$   
 $\frac{1}{C_T} = \frac{2}{4}$   
 $C_T = \frac{4}{2}$   
 $C_T = 2$

Type of circuit: COMBINED

Total Capacitance: 2 μF