

Name: My

Period: \_\_\_\_\_


Date: \_\_\_\_\_

Electric Circuits problems 1

SERIES	PARALLEL
$V = V_1 + V_2 + V_3$	$V = V_1 = V_2 = V_3$
$I = I_1 = I_2 = I_3$	$I = I_1 + I_2 + I_3$
$R = R_1 + R_2 + R_3$	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

I. Simplify the following electric circuits. Show your work to get full credit.

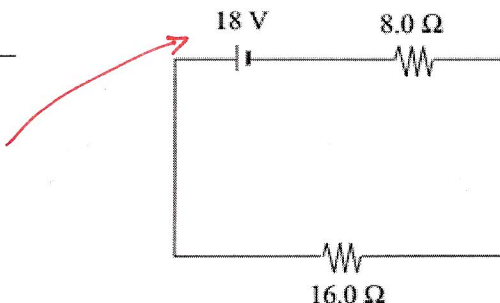
1.
  - a. Type of Circuit (Series/Parallel): Series
  - b. Total Resistance in the circuit: 24Ω
  - c. Current flowing in the circuit: 0.75A
  - d. Voltage for the 8Ω resistor: 6V
  - e. Voltage for the 16Ω resistor: 12V
  - f. Power dissipated by the 8Ω resistor: 4.5W
  - g. Power dissipated by the 16Ω resistor: 9W



b)  $R_T = R_1 + R_2 = 8 + 16 = 24\Omega$       d)  $V_1 = IR_1 = (0.75)(8\Omega) = 6V$   
 c)  $I = \frac{V}{R} = \frac{18V}{24\Omega} = 0.75A$        $V_2 = IR_2 = (0.75)(16\Omega) = 12V$

f)  $P = I^2R = (0.75)^2(8) = 4.5W$   
 $P = I^2R = (0.75)^2(16) = 9W$

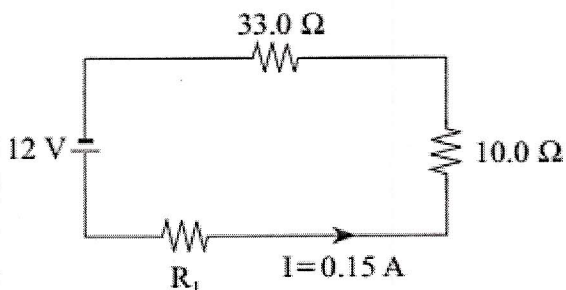2. What is the power dissipated in resistor R1 in the circuit shown in the diagram below?  $P =$  0.83W



step 2: Find Power

$P = I^2R = (0.15)^2(37)$

P = 0.83W

step 1: Find total Resistance in circuit


$R = \frac{V}{I} = \frac{12V}{.15} = 80\Omega$

In Series, the total resistance is added

$R_T = R_1 + R_2 + R_3$   
 $80 = R_1 + 10 + 33$

$80 = R_1 + 43$   
 $80 - 43 = R_1$   
 $R_1 = 37\Omega$

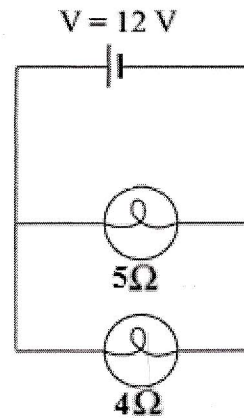- 3.
- Type of Circuit (Series/Parallel): Parallel
  - Total Resistance in the circuit: 2.22Ω
  - Current leaving the battery: 5.41 A
  - Current flowing through the 5 Ω resistor: 2.4 A
  - Current flowing through the 4 Ω resistor: 3 A
  - Voltage for the 5Ω resistor: 12V
  - Voltage for the 4 Ω resistor: 12V
  - Power dissipated by the 5Ω resistor: 28.8 W
  - Power dissipated by the 4Ω resistor: 36W



b)  $\frac{1}{R_T} = \frac{1}{5} + \frac{1}{4}$   
 $\frac{1}{R_T} = \frac{4+5}{20}$   
 $\frac{1}{R_T} = \frac{9}{20}$   
 $R_T = 20/9 = 2.22\Omega$

c)  $I = \frac{V}{R} = \frac{12}{2.22} = 5.41A$


d)  $I_1 = \frac{V}{R_1} = \frac{12}{5} = 2.4A$

e)  $I_2 = \frac{V}{R_2} = \frac{12}{4} = 3A$

w)  $P_1 = I_1^2 R_1 = (2.4)^2 (5) = 28.8W$

i)  $P_2 = I_2^2 R_2 = (3)^2 (4) = 36W$

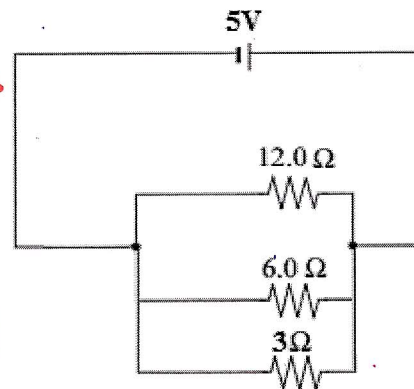- 4.
- Type of Circuit (Series/Parallel): Parallel
  - Total Resistance in the circuit: 1.71Ω
  - Current leaving the battery: 2.92A
  - Current flowing through the 12 Ω resistor: 0.42A
  - Current flowing through the 6 Ω resistor: 0.83A
  - Current flowing through the 3 Ω resistor: 1.67A
  - Voltage for the 12Ω resistor: 5V
  - Voltage for the 6 Ω resistor: 5V
  - Voltage for the 3 Ω resistor: 5V



b)  $\frac{1}{R_T} = \frac{1}{12} + \frac{1}{6} + \frac{1}{3}$   
 $\frac{1}{R_T} = \frac{1+2+4}{12}$   
 $\frac{1}{R_T} = \frac{7}{12}$   
 $R_T = \frac{12}{7} = 1.71\Omega$

c)  $I = \frac{V}{R} = \frac{5V}{1.71} = 2.92A$

d)  $I_1 = \frac{V}{R_1} = \frac{5V}{12} = 0.42A$

$I_2 = \frac{V}{R_2} = \frac{5}{6} = 0.83A$

$I_3 = \frac{V}{R_3} = \frac{5}{3} = 1.67A$