

Electricity: Combined Circuits

Name: \_\_\_\_\_ Period: 8th Date: \_\_\_\_\_

Combined Circuits


A combined circuit is one where their components are series-connected in some parts and parallel in others. We won't be able to apply a *single* set of rules to every part of that circuit [as we did in series and parallel].

Instead, we will have to identify which parts of that circuit are series and which parts are parallel, and then selectively apply series and parallel rules as necessary to simplify it to one equivalent (total) resistance.

SERIES	PARALLEL
$V = V_1 + V_2 + V_3$	$V = V_1 = V_2 = V_3$
$I = I_1 = I_2 = I_3$	$I = I_1 + I_2 + I_3$
$R = R_1 + R_2 + R_3$	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

$V = IR$   
 $P = I^2 R = IV$   
 $E = Pt$

Example 1: Complete the following table

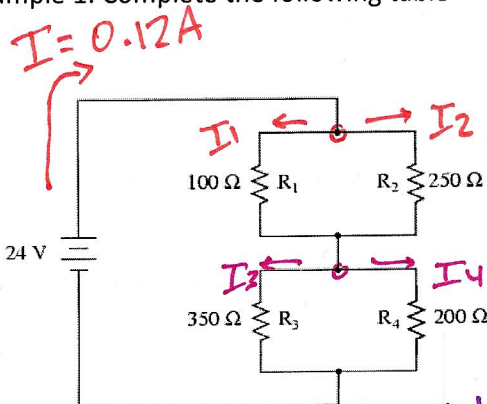

	$R_1$	$R_2$	$R_3$	$R_4$	Total	
V	8.57	8.57	15.27	15.27	24	Volts
I	.086	.034	.044	.076	.12	Amps
R	100	250	350	200	198.7	Ohms

STEP 1: Simplify Parallel sub-circuits

$\frac{1}{R_T} = \frac{1}{100} + \frac{1}{250}$   
 $\frac{1}{R_T} = \frac{5+2}{500}$   
 $\frac{1}{R_T} = \frac{7}{500}$

$\frac{1}{R_T} = \frac{1}{350} + \frac{1}{200}$   
 $\frac{1}{R_T} = \frac{4+7}{1400}$   
 $\frac{1}{R_T} = \frac{11}{1400}$

$R_T = \frac{500}{7} = 71.43 \Omega$

$R_T = \frac{1400}{11} = 127.27 \Omega$

STEP 2: Simplify in Series ( $R_{T1} + R_{T2}$ )

$R_T = R_{T1} + R_{T2} = 71.43 \Omega + 127.27 \Omega$

$R_T = 198.7 \Omega$

STEP 4: go back to Series & find  $V_1$  &  $V_2$



$V_1 = IR_{T1} = (.12A)(71.43) = 8.57V$

$V_2 = IR_{T2} = (.12A)(127.27) = 15.27V$

STEP 3: Find current in circuit

$I = \frac{V}{R_T} = \frac{24V}{198.7} = 0.12A$

STEP 5: Find current for each resistor

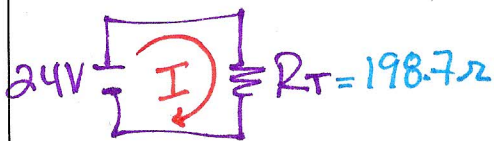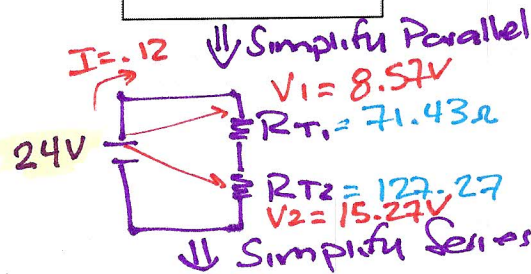

1. What is the overall current flowing in the circuit? 0.12

2. What is the current flowing through the  $R_4$  resistor? 0.076

3. What is the Power dissipated on the  $R_1$  resistor? 0.74W

$P = I_1 V_1 = (.086)(8.57)$   
 $P = 0.74W$

$I = \frac{V}{R_1} = \frac{8.57}{100}$   $I = \frac{V_2}{R_2} = \frac{8.57}{250}$   $I = \frac{V_3}{R_3} = \frac{15.27}{350}$   $I = \frac{V_4}{R_4} = \frac{15.27}{200}$   
 $I = 0.086A$   $I = 0.034A$   $I = 0.044A$   $I = 0.076A$

[I stays same]