




Electricity: Capacitors Quiz

Name: _____ Period: _____ Date: _____


I. Simplify the following electric circuits. Show your work to get full credit.

1.

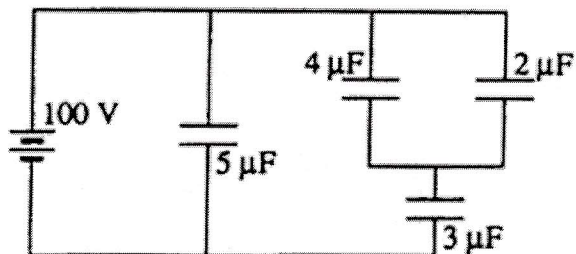


- a. Type of circuit: _____
- b. Total Capacitance in the circuit: _____

2.

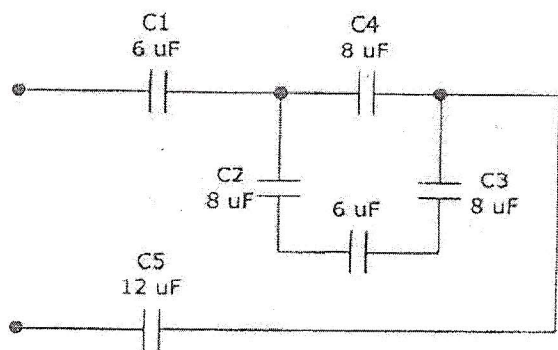

- a. Type of circuit: _____
- b. Total Capacitance in the circuit: _____
- c. Total charge in the circuit if the voltage provided is 120V _____

3.

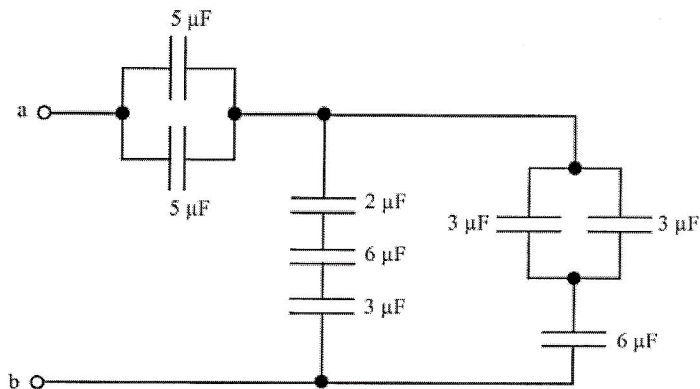

- a. Type of circuit: _____
- b. Total Capacitance in the circuit: _____

**II. Answer the following. Show work and provide final answer in scientific notation.**

1. A 6.5 nanofarad parallel plate capacitor holds a charge of magnitude $25\mu\text{C}$ on each plate.

a. What is the potential difference (Voltage) between the plates? _____

b. If the plates are separated by a distance of 0.45mm, what is the area of the plate? _____

c. What the electric potential energy (U) stored in the capacitor? _____

2. A capacitor is fully charged by a 16V battery and has $50\mu\text{J}$ oules of energy stored in it..

a. Find the charge on each conducting plate of the capacitor. _____

b. Find the value of the capacitance. _____

c. Find the separation of the plates is the surface area is 4.5mm^2 _____




Electricity: Capacitors Quiz

Name: Kly Period: _____ Date: _____

I. Simplify the following electric circuits. Show your work to get full credit.

1.

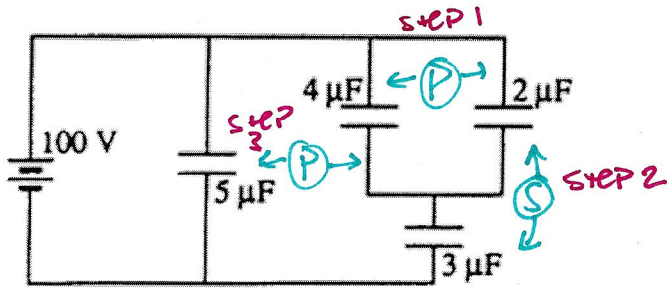

Ⓟ Parallel
Ⓢ Series

STEP 2


$$\frac{1}{C} = \frac{1}{6} + \frac{1}{3}$$

$$\frac{1}{C} = \frac{1+2}{6} = \frac{3}{6}$$

$$C = \frac{6}{3} = \underline{2\mu F}$$


- a. Type of circuit: Combined
- b. Total Capacitance in the circuit: 7 μF

2.

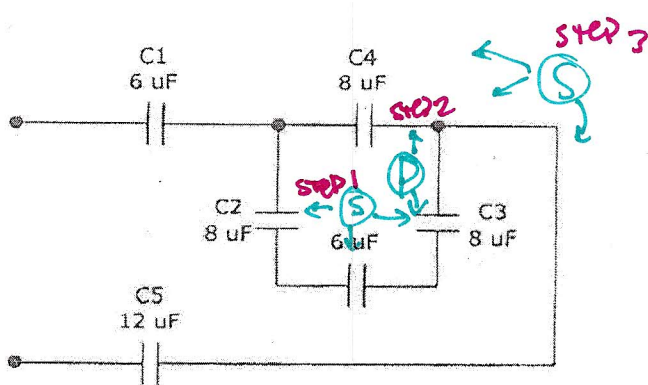

- a. Type of circuit: Combined
- b. Total Capacitance in the circuit: 2.89 μF
- c. Total charge in the circuit if the voltage provided is 120V 3.47 × 10⁻⁴ C

3.

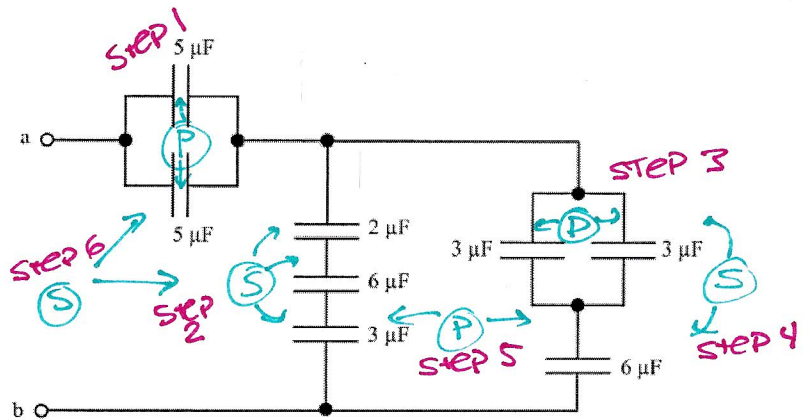

- a. Type of circuit: Combined
- b. Total Capacitance in the circuit: 2.86 μF

STEP 4

$$\frac{1}{C} = \frac{1}{6} + \frac{1}{6}$$

$$\frac{1}{C} = \frac{2}{6}$$

$$C = \frac{6}{2} = 3$$

STEP 2

$$\frac{1}{C} = \frac{1}{2} + \frac{1}{6} + \frac{1}{3}$$

$$\frac{1}{C} = \frac{3+1+2}{6}$$

$$\frac{1}{C} = \frac{6}{6}$$

$$C = 1$$

STEP 6

$$\frac{1}{C} = \frac{1}{10} + \frac{1}{4}$$

$$\frac{1}{C} = \frac{4+10}{40}$$

$$C = \frac{40}{14} = \underline{2.86}$$

c) $C = \frac{Q}{V}$

$Q = CV = (2.89 \times 10^{-6} \text{ F})(120)$

$Q = \underline{3.47 \times 10^{-4} \text{ C}}$



II. Answer the following. Show work and provide final answer in scientific notation.

1. A 6.5 nanofarad parallel plate capacitor holds a charge of magnitude $25\mu\text{C}$ on each plate.

a. What is the potential difference (Voltage) between the plates?

$$\underline{3.85 \times 10^3 \text{ V}}$$

b. If the plates are separated by a distance of 0.45mm, what is the area of the plate?

$$\underline{3.3 \times 10^{-1} \text{ F}}$$

c. What the electric potential energy (U) stored in the capacitor?

$$\underline{4.8 \times 10^{-2} \text{ J}}$$

$$C = 6.5 \times 10^{-9} \text{ F}$$

$$Q = 25 \times 10^{-6} \text{ C}$$

a) $V = ?$

$$a) C = \frac{Q}{V}$$

$$V = \frac{Q}{C} = \frac{25 \times 10^{-6}}{6.5 \times 10^{-9}} = 3846.15 = 3.85 \times 10^3 \text{ V}$$

b) $A = ?$

$$b) C = \frac{\epsilon_0 A}{d}$$

$$A = \frac{C \cdot d}{\epsilon_0} = \frac{(6.5 \times 10^{-9})(4.5 \times 10^{-4})}{8.85 \times 10^{-12}} = 0.33 = 3.3 \times 10^{-1} \text{ F}$$

c) $U = ?$

$$d = 0.45 \text{ mm} = 4.5 \times 10^{-4} \text{ m}$$

$$c) U = \frac{QV}{2} = \frac{(25 \times 10^{-6})(3.85 \times 10^3)}{2} = 4.8 \times 10^{-2} \text{ J}$$

2. A capacitor is fully charged by a 16V battery and has 50μJoules of energy stored in it..

a. Find the charge on each conducting plate of the capacitor.

$$\underline{6.25 \times 10^{-6} \text{ C}}$$

b. Find the value of the capacitance.

$$\underline{3.9 \times 10^{-7} \text{ F}}$$

c. Find the separation of the plates is the surface area is 4.5 mm^2

$$\underline{1.02 \times 10^{-10} \text{ m}}$$

$$V = 16 \text{ V}$$

$$U = 50 \times 10^{-6} \text{ J}$$

$$a) U = \frac{QV}{2}$$

$$Q = \frac{2U}{V} = \frac{2(50 \times 10^{-6})}{16} = 6.25 \times 10^{-6} \text{ C}$$

$$b) C = \frac{Q}{V} = \frac{6.25 \times 10^{-6}}{16} = 3.9 \times 10^{-7} \text{ F}$$

c)

$$A = 4.5 \text{ mm}^2 \left(\frac{1}{1000}\right)^2$$

$$A = 4.5 \times 10^{-6} \text{ m}^2$$

$$C = \frac{\epsilon_0 A}{d}$$

$$d = \frac{\epsilon_0 A}{C} = \frac{(8.85 \times 10^{-12})(4.5 \times 10^{-6})}{3.9 \times 10^{-7}}$$

$$d = \underline{1.02 \times 10^{-10} \text{ m}}$$