

Name: ky

Period: _____


Date: _____

Electricity: Capacitors Problems 2

SERIES	PARALLEL	
$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$	$C_T = C_1 + C_2 + \dots$	
$C = \frac{Q}{V}$	$C = \epsilon_0 \frac{A}{d}$	$U = \frac{1}{2} Q \Delta V = \frac{1}{2} C V^2$

I. Simplify the following electric circuits and answer the following.


1.

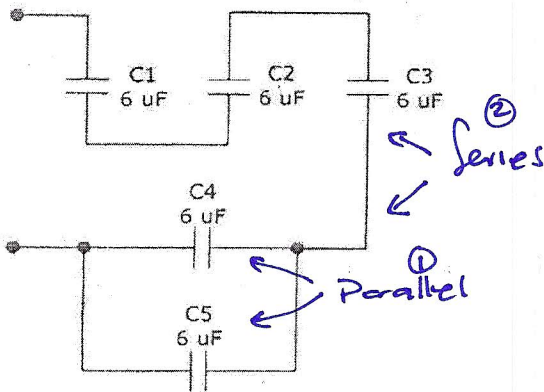

Type of circuit: COMBINED

Total Capacitance: $12/7 \mu F = 1.71 \mu F$


2.

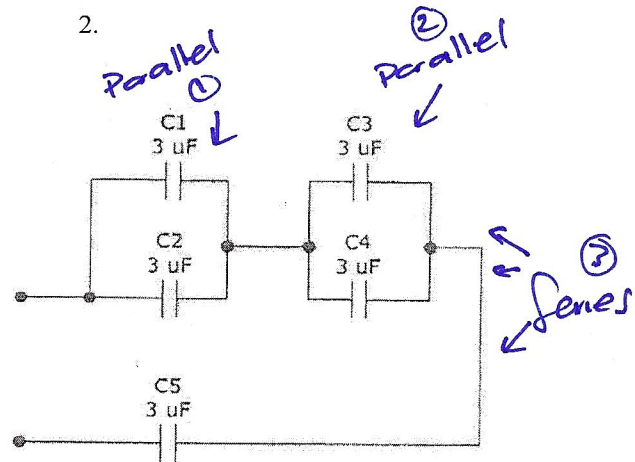

Type of circuit: COMBINED

Total Capacitance: $3/2 \mu F = 1.5 \mu F$


3.

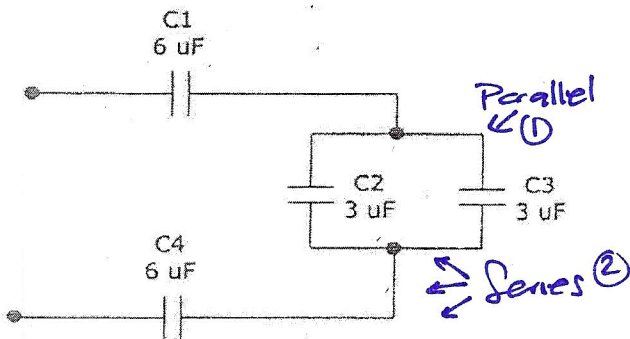

Type of circuit: COMBINED

Total Capacitance: $2 \mu F$


4.

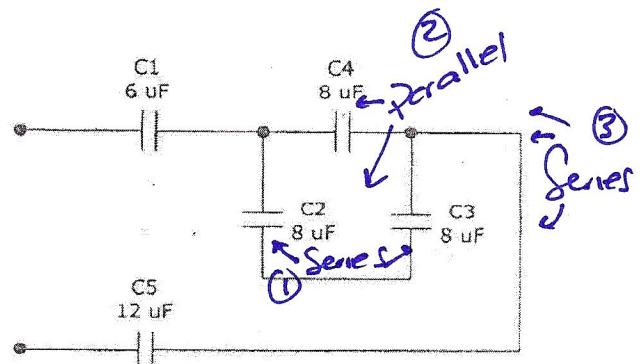

Type of circuit: COMBINED

Total Capacitance: $3 \mu F$


5.

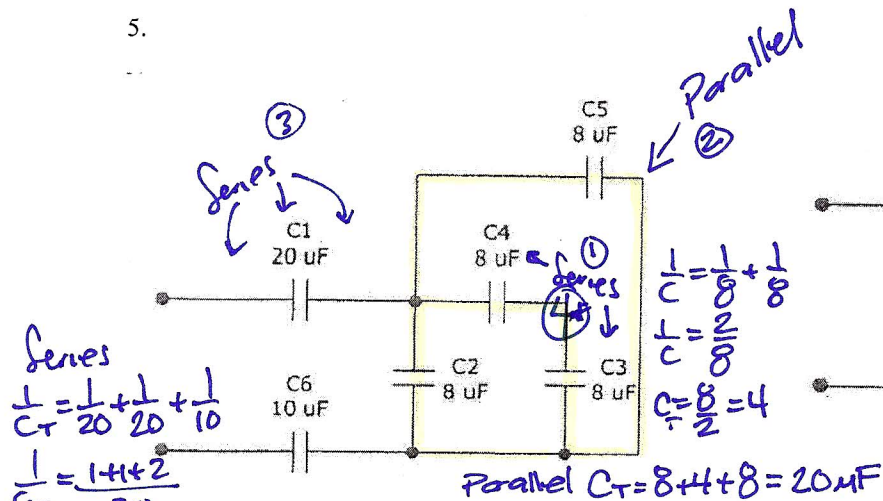

Type of circuit: Combined

Total Capacitance: 5 uF


6.

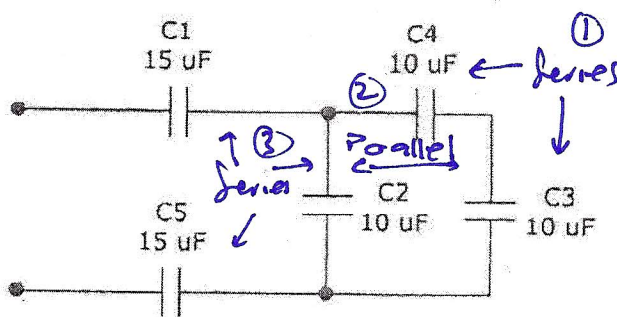

Type of circuit: Combined

Total Capacitance: 5 uF


7.

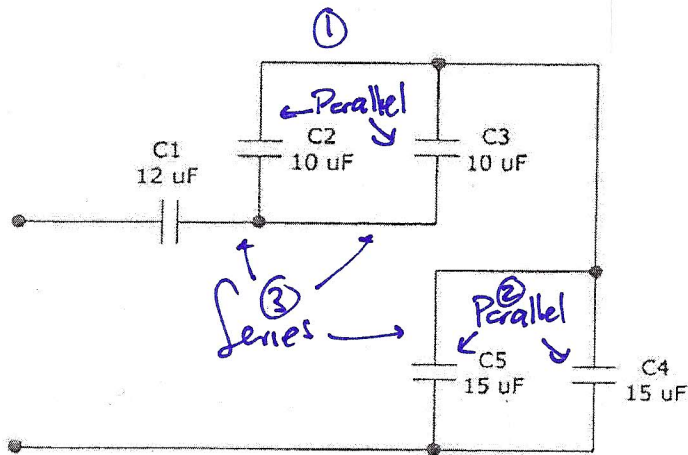

Type of circuit: Combined

Total Capacitance: 6 uF

8.

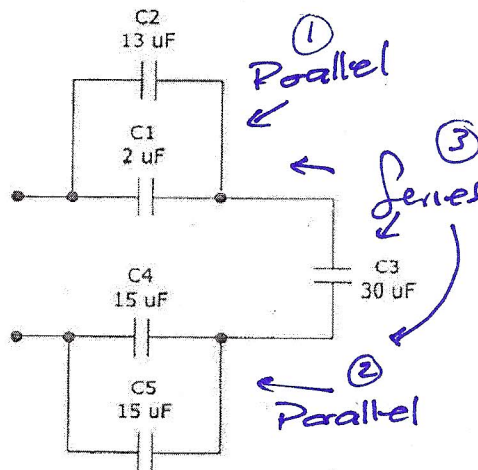


Type of circuit: Combined


Total Capacitance: $\frac{30}{4} \mu F = 7.5 \mu F$

Electric Potential & Capacitors II


1.

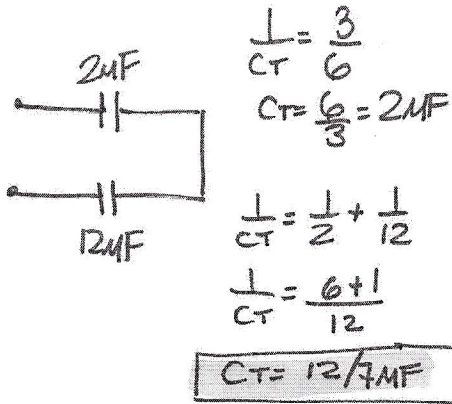


2.

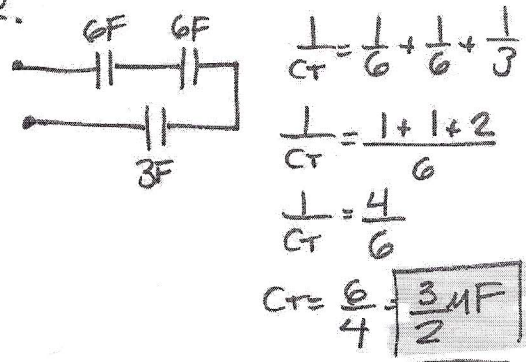




3.

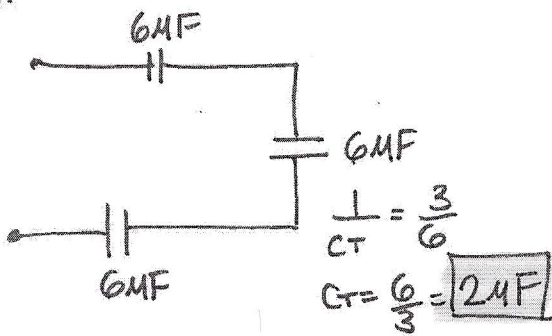




4.

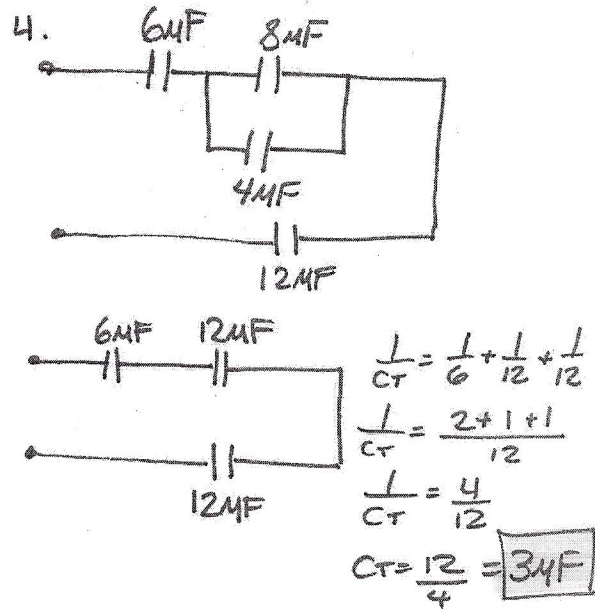

5.

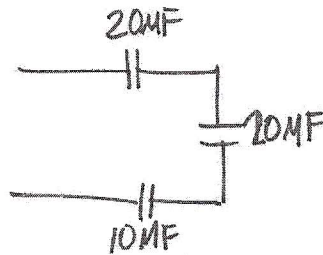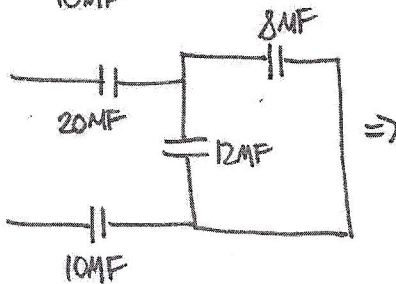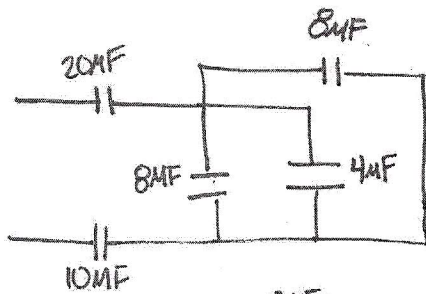

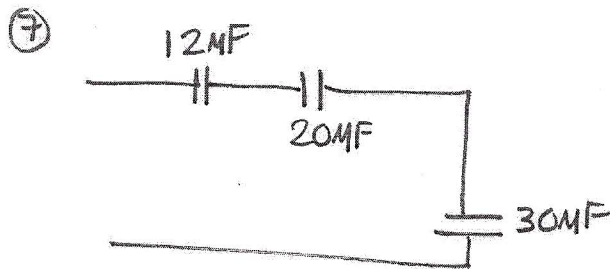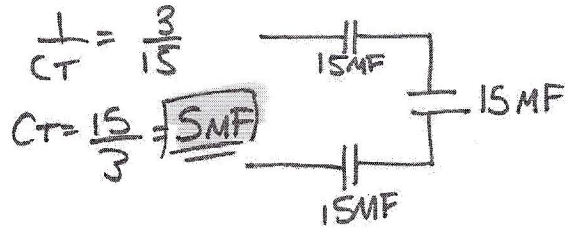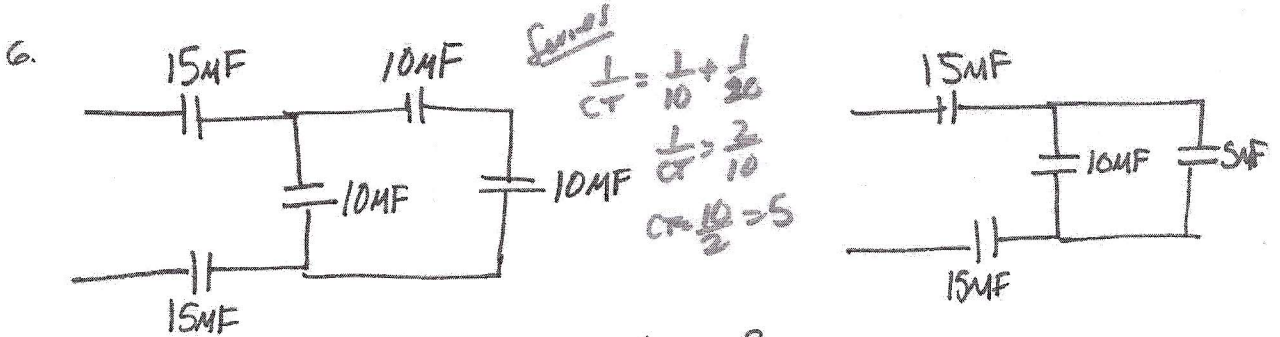
$\frac{1}{C_T} = \frac{1}{20} + \frac{1}{20} + \frac{1}{10}$
 $\frac{1}{C_T} = \frac{1+1+2}{20}$
 $\frac{1}{C_T} = \frac{4}{20}$
 $C_T = \frac{20}{4} = 5\mu F$



$$\frac{1}{C_T} = \frac{1}{12} + \frac{1}{20} + \frac{1}{30}$$

$$\frac{1}{C_T} = \frac{5+3+2}{60}$$
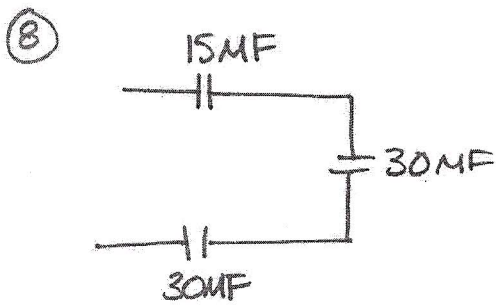
$$\frac{1}{C_T} = \frac{10}{60} \quad \boxed{C_T = 6MF}$$



$$\frac{1}{C_T} = \frac{1}{15} + \frac{1}{30} + \frac{1}{30}$$

$$\frac{1}{C_T} = \frac{2+1+1}{30}$$

$$\boxed{C_T = \frac{30}{4} = 7.5MF}$$

II. Answer the following. Show all your work

1. A 8 nanofarad parallel plate capacitor holds a charge of magnitude $45\mu\text{C}$ on each plate.
 a. What is the potential difference between the plates?
 b. If the plates are separated by a distance of 0.2mm, what is the area of the plate?
 c. What the electric potential energy stored in the capacitor?

c) $U = \frac{1}{2} QV$
 $U = \frac{1}{2} (45 \times 10^{-6}) (5625)$
 $U = 0.126 \text{ J}$

$C = 8 \text{ nF} = 8 \times 10^{-9} \text{ F}$
 $Q = 45 \mu\text{C} = 45 \times 10^{-6} \text{ C}$

a) $C = \frac{Q}{V}$


$V = \frac{Q}{C} = \frac{45 \times 10^{-6} \text{ C}}{8 \times 10^{-9} \text{ F}} = 5625 \text{ V}$

b) $C = \frac{\epsilon_0 A}{d}$

$A = \frac{Cd}{\epsilon_0} = \frac{(8 \times 10^{-9}) (0.0002)}{8.85 \times 10^{-12}} = 0.18 \text{ m}^2$

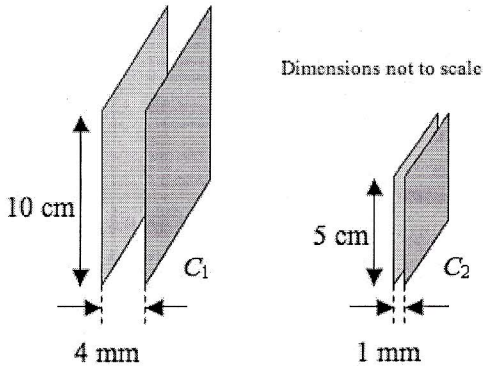2. Capacitor C1 consists of square parallel plates 10cm on a side, and separated by a distance of 4mm, as shown. Capacitor C2 has squared parallel plates 5cm on a side, and separated by a distance of 1mm.
 a. What is the capacitance of the first capacitor?
 b. What is the capacitance of the second capacitor
 c. What is the ratio between the capacitances of the two parallel-plate systems? [$C_1:C_2$]

$\frac{2.21 \times 10^{-11} \text{ F}}{2.21 \times 10^{-11} \text{ F}} = 1$



a. $C_1 = \frac{\epsilon_0 A}{d} = \frac{(8.85 \times 10^{-12}) [(0.1)(0.1)]}{(0.004)} = 2.21 \times 10^{-11} \text{ F}$

b. $C_2 = \frac{\epsilon_0 A}{d} = \frac{(8.85 \times 10^{-12}) [(0.05)(0.05)]}{(0.001)} = 2.21 \times 10^{-11} \text{ F}$

$\frac{C_1}{C_2} = \frac{2.21 \times 10^{-11}}{2.21 \times 10^{-11}} = 1$

3. A capacitor is fully charged by a 10V battery and has 20miliJoules of energy stored in it..
 a. Find the charge on each conducting plate of the capacitor.
 b. Find the value of the capacitance.
 c. Find the separation of the plates is the surface area is 2.5 mm^2

$\frac{4 \times 10^{-3} \text{ C}}{4 \times 10^{-4} \text{ F}} = 5.53 \times 10^{-14} \text{ m}$

$V = 10 \text{ V}$
 $U = 20 \text{ mJ} = 20 \times 10^{-3} \text{ J}$

b) $C = \frac{Q}{V} = \frac{4 \times 10^{-3}}{10 \text{ V}} = 4 \times 10^{-4} \text{ F}$

a) $U = \frac{1}{2} QV$

$Q = \frac{2U}{V} = \frac{2(20 \times 10^{-3})}{10}$

$Q = 0.004 \text{ C} = 4 \times 10^{-3} \text{ C}$

c) $C = \frac{\epsilon_0 A}{d}$

$= 2.5 \text{ mm}^2 \left(\frac{1 \text{ m}}{1000 \text{ mm}} \right)^2$
 $= 2.5 \times 10^{-6} \text{ m}^2$

$d = \frac{\epsilon_0 A}{C} = \frac{(8.85 \times 10^{-12}) (2.5 \times 10^{-6})}{4 \times 10^{-4}} = 5.53 \times 10^{-14} \text{ m}$