


Name: Play Period: _____ Date: _____

Electricity: Combined Electric Circuits problems 2


SERIES	PARALLEL	$V=I/R$
$V=V_1+V_2+V_3$	$V=V_1=V_2=V_3$	
$I=I_1=I_2=I_3$	$I=I_1 + I_2 + I_3$	
$R=R_1+R_2+R_3$	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$	$P=IV=I^2R$

I. Simplify the following electric circuits and answer the following. Show your work to get full credit. You might need to work the problems in a different sheet of paper.


1.

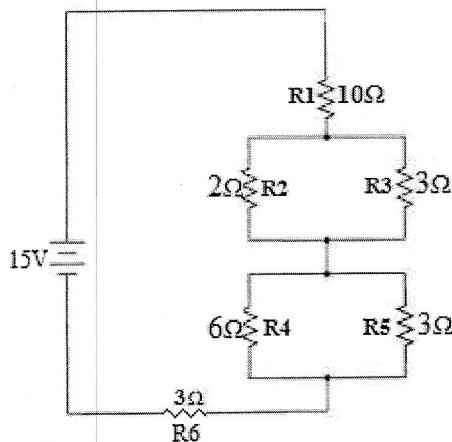a. Total Resistance in the circuit: 16.2 Ωb. Current flowing in the circuit: 0.93Ac. Voltage V_1 9.3V V_2 1.12V V_3 1.12V V_4 1.86V V_5 1.86V V_6 2.79Vd. Current I_1 0.93A I_2 0.56A I_3 0.37A I_4 0.31A I_5 0.62A I_6 0.93A

2.

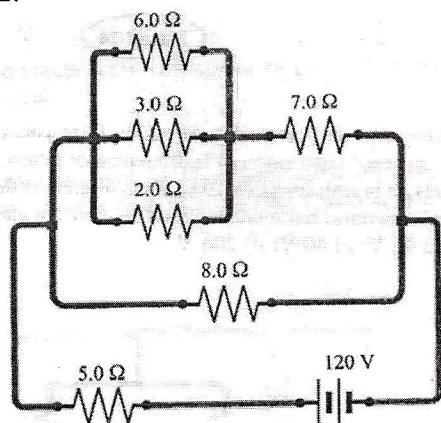a. Total Resistance in the circuit: 9Ωb. Current flowing in the circuit: 13.33Ac. Voltage on the 8Ω resistor: 53.32Vd. Voltage on the 3Ω resistor: 6.67Ve. Current on the 6Ω resistor: 1.11Af. Current on the 7Ω resistor: 6.67Ag. Current on the 5Ω resistor: 13.33A

3.

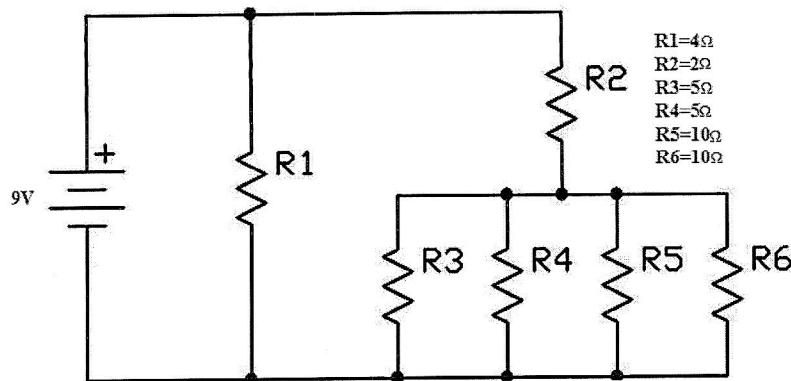

a. Total Resistance in the circuit: 1.91Ω


b. Current flowing in the circuit: 4.71A

c. Voltage
V1 9V V2 4.9V V3 4.09V V4 4.09V V5 4.09V V6 4.09V

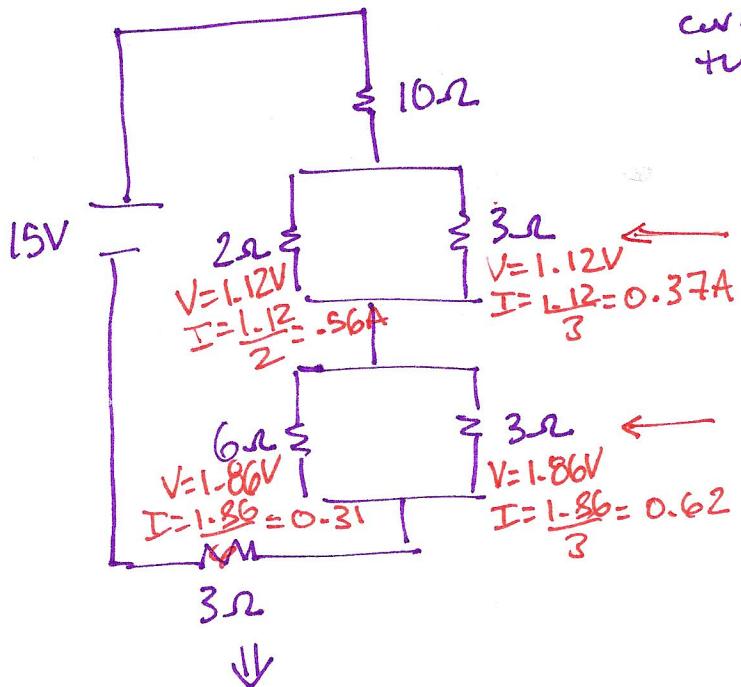d. Current
I1 2.25A I2 2.45A I3 0.82A I4 0.82A I5 0.41A I6 0.41A

①

- Step 1: Simplify diagrams
 Step 2: Find total resistance
 Step 3: Find total current
 Step 4: Go back & split voltage & current [depending on type of circuit]



Simplify Parallel

$$\frac{1}{R_T} = \frac{1}{2} + \frac{1}{3} \quad \frac{1}{R_T} = \frac{5}{6}$$

$$\frac{1}{R_T} = \frac{3+2}{6} \quad R_T = 6 / 5 = 1.2$$


Simplify Parallel

$$\frac{1}{R_T} = \frac{1}{6} + \frac{1}{3}$$

$$\frac{1}{R_T} = \frac{1+2}{6}$$

$$\frac{1}{R_T} = \frac{3}{6}$$

$$R_T = \frac{6}{3} = 2\Omega$$

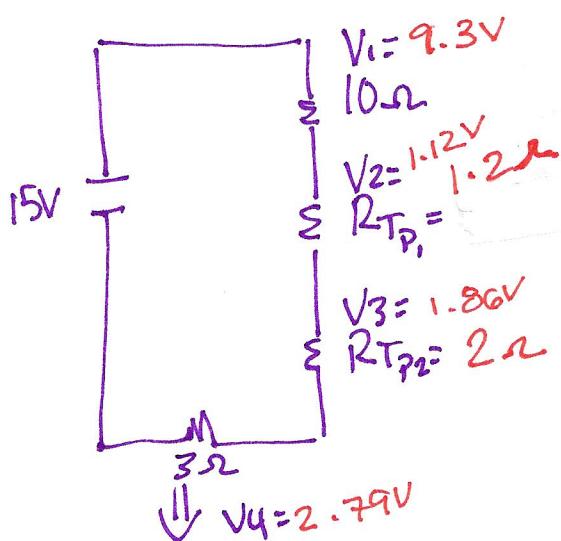

Series

$$R_T = 10 + 1.2 + 2 + 3$$

$$R_T = 16.2\Omega$$


To find voltage split

$$V_1 = IR_1 = (.93A)(10) = 9.3V$$

$$V_2 = IR_{T2} = (.93A)(1.2) = 1.12V$$

$$V_3 = IR_{T2} = (.93A)(2) = 1.86V$$


$$V_4 = IR_4 = (.93)(3) = 2.79V$$

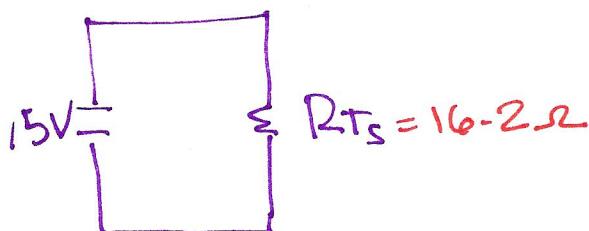

TOTAL Current

$$I = \frac{V}{R_T} = \frac{15}{16.2} = 0.93A$$

$$\textcircled{2} \quad V = 6.67V$$

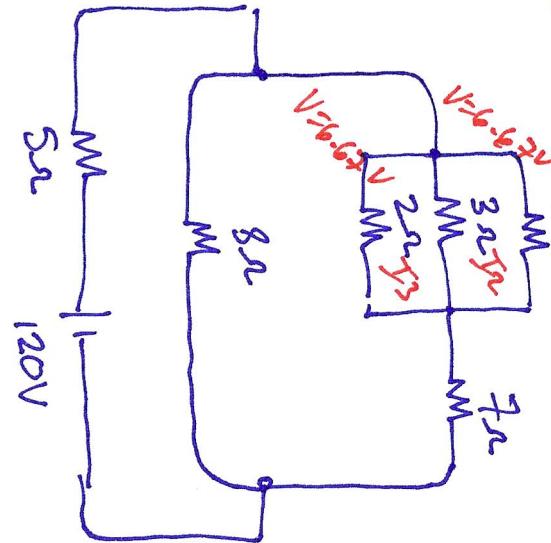


$$\begin{aligned} R_{TP} &= \frac{1}{\frac{1}{6} + \frac{1}{3} + \frac{1}{2}} \\ \frac{1}{R_{TP}} &= \frac{1+2+3}{6} \\ R_{TP} &= \frac{6}{6} = 1\Omega \end{aligned}$$

$$\begin{aligned} I_1 &= \frac{V}{R} = \frac{6.67}{6} = 1.11A \\ I_2 &= \frac{V}{R} = \frac{6.67}{3} = 2.22A \\ I_3 &= \frac{V}{R} = \frac{6.67}{2} = 3.33A \end{aligned}$$

Simplify
Circuit to
Find total
Resistance


$$\begin{aligned} R_{TS} &= 1 + 7 \\ R_{TS} &= 2\Omega \end{aligned}$$
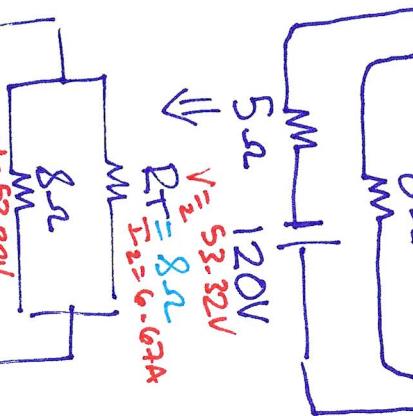
$$\begin{aligned} I_1 &= \frac{V}{R} = \frac{6.67}{12} = 0.55A \\ I_2 &= \frac{V}{R} = \frac{6.67}{8} = 0.83A \\ I_3 &= \frac{V}{R} = \frac{6.67}{7} = 0.95A \end{aligned}$$



$$\begin{aligned} \frac{1}{R_{TP}} &= \frac{1}{8} + \frac{1}{8} \\ \frac{1}{R_{TP}} &= \frac{2}{8} \\ R_{TP} &= \frac{8}{2} = 4\Omega \end{aligned}$$
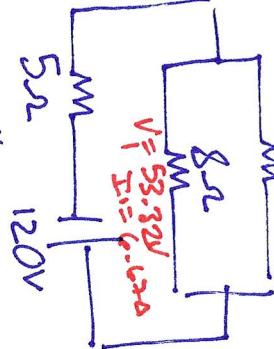
$$\begin{aligned} I_1 &= \frac{V}{R} = \frac{53.32}{8} = 6.67A \\ I_2 &= \frac{V}{R} = \frac{53.32}{8} = 6.67A \\ I_3 &= \frac{V}{R} = \frac{53.32}{8} = 6.67A \end{aligned}$$



$$\begin{aligned} \frac{V_2}{R_{TP}} &= 53.32V \\ R_{TP} &= 4\Omega \end{aligned}$$


$$R_{TP} = 4 + 5 = 9\Omega$$

$$I = \frac{V}{R} = \frac{120}{9} = 13.33A$$

$$\begin{aligned} V_1 &= (13.33)(5) = 66.65V \\ V_2 &= (13.33)(4) = 53.32V \end{aligned}$$

$$\begin{aligned} \frac{V_1}{R_{TP}} &= 66.65V \\ R_{TP} &= 5\Omega \\ 5\Omega &= 120V \end{aligned}$$

(3)

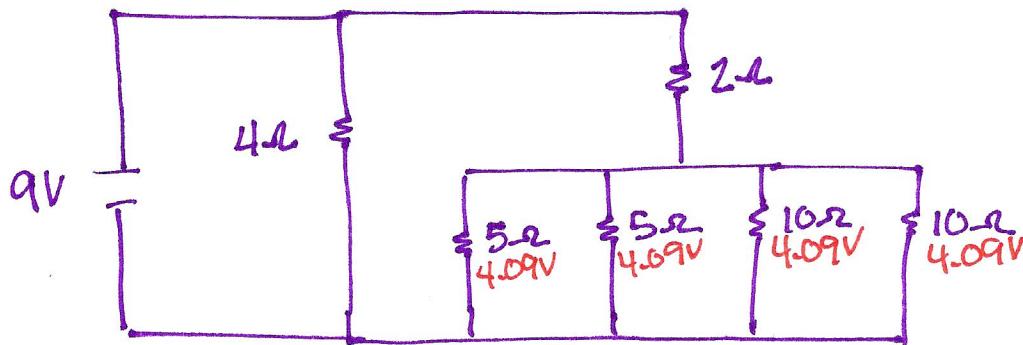

$$I_s = \frac{4.09}{5} = 0.82$$

$$I_4 = \frac{4.09}{5} = 0.82$$



$$I_5 = \frac{4.09}{10} = 0.41$$

$$I_6 = \frac{4.09}{10} = 0.41$$

 \Downarrow Simplify Parallel

$$\frac{1}{R_T} = \frac{1}{5} + \frac{1}{5} + \frac{1}{10} + \frac{1}{10}$$

$$R_T = 1.67 \Omega$$

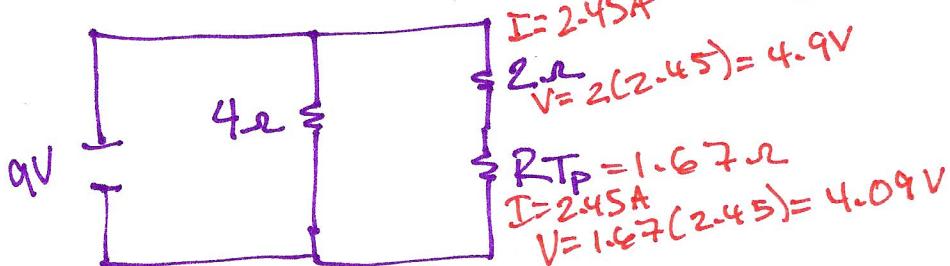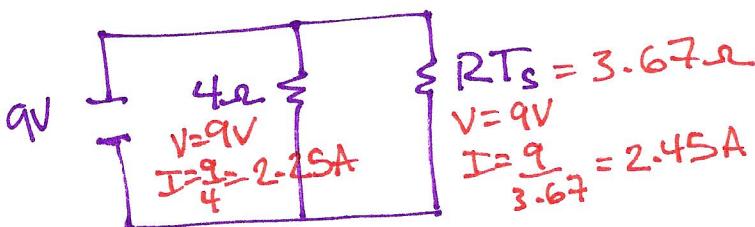 \Downarrow Simplify Series \Downarrow Simplify Parallel